

CPU with Five-Stage MIPS Pipeline

Zhijian LIU

September 8, 2016

Course: Computer System
Instructor: Professor Alei Liang
Teaching Assistant: Shusheng He

Contents

| | |
|------------------------------------|----------|
| 1 Introduction | 2 |
| 2 Main Modules | 2 |
| 2.1 Stage Modules | 2 |
| 2.1.1 Instruction Fetch | 2 |
| 2.1.2 Instruction Decode | 3 |
| 2.1.3 Execution | 4 |
| 2.1.4 Memory Access | 5 |
| 2.1.5 Write Back | 6 |
| 2.2 Latch Modules | 6 |
| 2.3 Storage Modules | 6 |
| 2.3.1 Instruction ROM | 6 |
| 2.3.2 Data RAM | 7 |
| 2.3.3 Register File | 7 |
| 2.4 Control Module | 7 |
| 3 Test Summary | 7 |
| 3.1 Test Case | 7 |
| 4 Acknowledgements | 8 |

1 Introduction

This report is a detailed summary on the final project of the "Computer System" course. In this project, I implemented a toy CPU with five-stage MIPS pipeline. The project has the following features:

- It supports almost all of the MIPS standard integer instructions (except those related to the coprocessors).
- It supports the full bypassing in order to mitigate the data hazards.
- It supports the automatic testing.

The project is written in Verilog HDL and is available under the open-source MIT License at <https://github.com/zhijian-liu/mips-cpu>.

2 Main Modules

2.1 Stage Modules

In the five-stage MIPS pipeline, there are obviously five separate pipeline stages:

- stage IF (instruction fetch)
- stage ID (instruction decode)
- stage EX (execution)
- stage MEM (memory access)
- stage WB (write back)

In my design philosophy, each of them should be implemented as a single module.

2.1.1 Instruction Fetch

The main function of this module is to maintain the program counter and send it to the instruction ROM in order to fetch the current instruction.

| Interface | Type | Usage |
|--------------------------|------|--------------|
| clock | in | clock signal |
| reset | in | reset signal |
| stall | in | stall signal |
| register_pc_read_data | out | register PC |
| register_pc_write_enable | in | |
| register_pc_write_data | in | |

Table 1: the interfaces of the stage IF

This module is implemented in `src/cpu/stage/stage_if.v`.

2.1.2 Instruction Decode

The main function of this module is to decode the instruction and extract the operator, category, operands and destination from it.

| Interface | Type | Usage |
|----------------------------|------|------------------------------------|
| reset | in | reset signal |
| instruction_i | in | instruction |
| instruction_o | out | |
| operator | out | operator |
| category | out | category of the operator |
| operand_a | out | operands |
| operand_b | out | |
| register_read_enable_a | out | read port A of the register file |
| register_read_address_a | out | |
| register_read_data_a | in | |
| register_read_enable_b | out | read port B of the register file |
| register_read_address_b | out | |
| register_read_data_b | in | |
| register_write_enable | out | write port of the register file |
| register_write_address | out | |
| register_write_data | out | |
| register_pc_read_data | in | register PC |
| register_pc_write_enable | out | |
| register_pc_write_data | out | |
| ex_operator | in | data forwarding from the stage EX |
| ex_register_write_enable | in | |
| ex_register_write_address | in | |
| ex_register_write_data | in | |
| mem_register_write_enable | in | data forwarding from the stage MEM |
| mem_register_write_address | in | |
| mem_register_write_data | in | |
| stall_request | out | whether or not is to request stall |

Table 2: the interfaces of the stage ID

In order to mitigate the data hazards¹, some interfaces are designed to fetch the latest data forwarding² from the stage EX and the stage MEM.

After implementing the full bypassing, there is only one kind of data hazard: a load instruction immediately followed by an instruction which has data dependency on it. In this case, we have to enable the "stall_request" signal in order to stall the pipeline for one cycle.

This module is implemented in `src/cpu/stage/stage_id.v`.

¹[https://en.wikipedia.org/wiki/Hazard_\(computer_architecture\)#Data_hazards](https://en.wikipedia.org/wiki/Hazard_(computer_architecture)#Data_hazards)

²https://en.wikipedia.org/wiki/Operand_forwarding

2.1.3 Execution

The main function of this module is to calculate the operation result according to the operator and operands received from the stage ID.

| Interface | Type | Usage |
|------------------------------|------|------------------------------------|
| reset | in | reset signal |
| instruction_i | in | instruction |
| instruction_o | out | |
| operator_i | in | operator |
| operator_o | out | |
| category | in | sub-category of the operator |
| operand_a_i | in | operands |
| operand_a_o | out | |
| operand_b_i | in | |
| operand_b_o | out | |
| register_write_enable_i | in | write port of the register file |
| register_write_enable_o | out | |
| register_write_address_i | in | |
| register_write_address_o | out | |
| register_write_data_i | in | |
| register_write_data_o | out | |
| register_hi_write_enable | out | register HI |
| register_hi_write_data | out | register LO |
| register_lo_write_enable | out | |
| register_lo_write_data | out | data forwarding from the stage MEM |
| mem_register_hi_write_enable | in | |
| mem_register_hi_write_data | in | |
| mem_register_lo_write_enable | in | |
| mem_register_lo_write_data | in | data forwarding from the stage WB |
| wb_register_hi_read_data | in | |
| wb_register_hi_write_enable | in | |
| wb_register_hi_write_data | in | |
| wb_register_lo_read_data | in | |
| wb_register_lo_write_enable | in | |
| wb_register_lo_write_data | in | |
| stall_request | out | whether or not is to request stall |

Table 3: the interfaces of the stage EX

In order to mitigate the data hazards, some interfaces are designed to fetch the latest data forwarding from the stage MEM and the stage WB.

Note that the "stall_request" signal is actually redundant because in the functional simulation³, all kinds of calculation can be finished in a single cycle.

This module is implemented in `src/cpu/stage/stage_ex.v`.

³https://en.wikipedia.org/wiki/Logic_simulation

2.1.4 Memory Access

The main function of this module is to handle the memory access instruction: calculate the effective memory address⁴ and send it to the data RAM in order to execute the load or store operation.

| Interface | Type | Usage |
|----------------------------|------|---------------------------------|
| reset | in | reset signal |
| instruction | in | instruction |
| operator | in | operator |
| operand_a | in | operands |
| operand_b | in | |
| memory_read_enable | out | read port of the data RAM |
| memory_read_address | out | |
| memory_read_data | in | |
| memory_write_enable | out | write port of the data RAM |
| memory_write_address | out | |
| memory_write_select | out | |
| memory_write_data | out | |
| register_write_enable_i | in | write port of the register file |
| register_write_enable_o | out | |
| register_write_address_i | in | |
| register_write_address_o | out | |
| register_write_data_i | in | |
| register_write_data_o | out | |
| register_hi_write_enable_i | in | register HI |
| register_hi_write_enable_o | out | |
| register_hi_write_data_i | in | |
| register_hi_write_data_o | out | |
| register_lo_write_enable_i | in | register LO |
| register_lo_write_enable_o | out | |
| register_lo_write_data_i | in | |
| register_lo_write_data_o | out | |

Table 4: the interfaces of the stage MEM

This module is implemented in `src/cpu/stage/stage_mem.v`.

⁴<https://www.cs.umd.edu/class/sum2003/cmsc311/Notes/Mips/addr.html>

2.1.5 Write Back

The main function of this module is to maintain the register HI and register LO.

| Interface | Type | Usage |
|--------------------------|------|--------------|
| clock | in | clock signal |
| reset | in | reset signal |
| register_hi_read_data | out | register HI |
| register_hi_write_enable | in | |
| register_hi_write_data | in | |
| register_lo_read_data | out | register LO |
| register_lo_write_enable | in | |
| register_lo_write_data | in | |

Table 5: the interfaces of the stage WB

This module is implemented in `src/cpu/stage/stage_wb.v`.

2.2 Latch Modules

In the five-stage MIPS pipeline, there are totally four pipeline latches which act as the buffers between the neighbouring pipeline stages.

These modules are implemented in:

- `src/cpu/latch/latch_if_id.v`
- `src/cpu/latch/latch_id_ex.v`
- `src/cpu/latch/latch_ex_mem.v`
- `src/cpu/latch/latch_mem_wb.v`

Note that all of the pipeline latches propagate the data on the rising edge of the clock signal.

2.3 Storage Modules

In my implementation, all of the storage modules write the data on the falling edge of the clock signal. Otherwise, some additional codes will be needed to support the bypassing inside the storage modules.

2.3.1 Instruction ROM

Because the instructions cannot be modified at runtime, the instruction ROM has only one major function: memory read. It uses a set of input wires to read the program counter and outputs the corresponding instruction.

This module is implemented in `src/rom.v`.

2.3.2 Data RAM

Unlike the instruction ROM, the data RAM has two major functions: memory read and memory write. It uses a set of input wires to read the address and outputs the corresponding data. At the meantime, it also provides a set of wires for writing. This module is implemented in `src/ram.v`.

2.3.3 Register File

The register file provides two sets of input wires for querying the value of a given register, and a set of wires for writing a register. This module is implemented in `src/cpu/register.v`.

2.4 Control Module

The main function of the control module is to receive the stall request from the pipeline stages and send the stall signal to the pipeline latches. This module is implemented in `src/cpu/control.v`.

3 Test Summary

3.1 Test Case

There are nine test cases in total:

- `test/test-logic`: check the logical instructions.
- `test/test-shift`: check the shift instructions.
- `test/test-move`: check the move instructions.
- `test/test-arithmetic`: check the arithmetic instructions.
- `test/test-jump`: check the jump instructions.
- `test/test-branch`: check the branch instructions.
- `test/test-memory`: check the memory instructions.
- `test/test-stall`: check the stall detection.
- `test/test-forwarding`: check the data forwarding.

In each test folder, there are totally three files:

- `asm.s`: the testing MIPS assembly code.
- `test.v`: the automatic testing code written in Verilog HDL.
- `Makefile`: the testing script.

A detailed guide to running the automatic test is written in `README.md`.

4 Acknowledgements

I would like to thank Professor Alei Liang for bringing me such a wonderful course, Shusheng He for his hard work and warm devotion, and Yurong You, Zihao Ye and Lequn Chen for valuable discussions.